

# RLC Circuits

Pablo M. Olmos ([olmos@tsc.uc3m.es](mailto:olmos@tsc.uc3m.es))

Emilio Parrado ([emipar@tsc.uc3m.es](mailto:emipar@tsc.uc3m.es))

March 14, 2018

**uc3m**

# Index

1 General solution of the Second-order differential equation

2 RLC circuits

3 RLC circuits as systems (filters)

## Second order linear differential equation with constant coefficients

Compute  $y(t)$  such that  $y(t_0) = y_0$ ,  $\frac{dy(t)}{dt}|_{t=t_0} = y_1$  if

$$\frac{d^2y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_0^2 y(t) = \gamma$$

where  $\alpha, \omega_0^2$  are real constants.

## Second order linear differential equation with constant coefficients

Compute  $y(t)$  such that  $y(t_0) = y_0$ ,  $\frac{dy(t)}{dt}|_{t=t_0} = y_1$  if

$$\frac{d^2y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_0^2 y(t) = \gamma$$

where  $\alpha$ ,  $\omega_0^2$  are real constants.

**Characteristic equation:**

$s_1$  and  $s_2$  are the roots of the equation

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Thus

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

**Case  $\alpha > \omega_0$ :  $s_1$  and  $s_2$  are negative real constants**

$$y(t) = A_1 e^{s_1(t-t_0)} + A_2 e^{s_2(t-t_0)} + \frac{\gamma}{\omega_0^2} \quad t \geq t_0,$$

where  $A_1$  and  $A_2$  can be found using the initial conditions.

## Exercise

Let  $x(t) = 3u(t)$  be the input signal to a system defined by the following input/output relationship:

$$\frac{d^2y(t)}{dt^2} + 6\frac{dy(t)}{dt} + 5y(t) = x(t),$$

where  $y(t)$  is the output signal. If we know that  $y(0) = 0$  and  $\frac{dy(t)}{dt}|_{t=0} = 0$ , compute and plot  $y(t)$ .

**Sol.**


For  $t \geq 0$ , the equation that gives the output is a second-order differential equation of the form

$$\frac{d^2y(t)}{dt^2} + 6\frac{dy(t)}{dt} + 5y(t) = 3 \quad t \geq 0$$

$$s^2 + 6s + 5 = 0 \Rightarrow s_1 = -3 + \sqrt{9-5} = -1, s_2 = -3 - \sqrt{2} = -5$$

$$y(t) = A_1 e^{-t} + A_2 e^{-5t} + \frac{3}{5} \quad t \geq 0$$

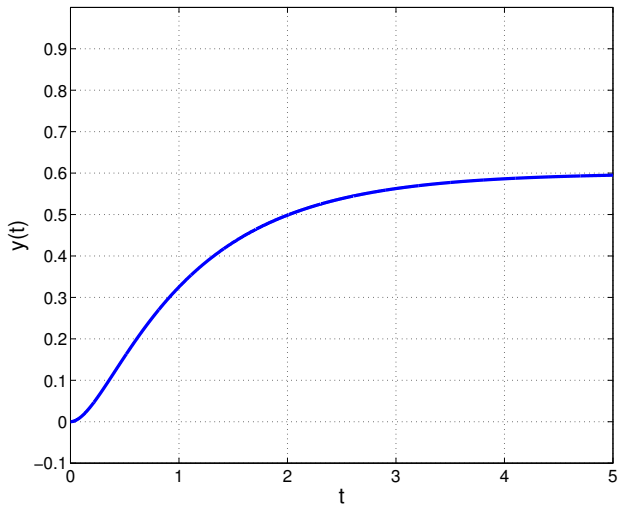Using the initial conditions we find  $A_1 = \frac{-3}{5}$  and  $A_2 = \frac{3}{25}$ .



The response of this system to the unit step is said to be *overdamped*.



Case  $\alpha < \omega_0$ :  $s_1$  and  $s_2$  are complex

$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \quad s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

Define  $\omega_d \doteq \sqrt{\omega_0^2 - \alpha^2}$ .

$$y(t) = B_1 e^{-\alpha(t-t_0)} \cos(\omega_d(t-t_0)) + B_2 e^{-\alpha(t-t_0)} \sin(\omega_d(t-t_0)) + \frac{\gamma}{\omega_0^2} \quad t \geq t_0,$$

where  $B_1$  and  $B_2$  can be found using the initial conditions.

$\alpha = 0$

Oscillation around  $\gamma/\omega_0^2$ !! The solution **does not** converge to a constant value in the limit  $t \rightarrow \infty$ !!!

## Exercise

Let  $x(t) = 3u(t)$  be the input signal to a system defined by the following input/output relationship:

$$\frac{d^2y(t)}{dt^2} + \frac{dy(t)}{dt} + 5y(t) = x(t),$$

where  $y(t)$  is the output signal. If we know that  $y(0) = 0$  and  $\frac{dy(t)}{dt}|_{t=0} = 0$ , compute and plot  $y(t)$ .

**Sol.**


For  $t \geq 0$ , the equation that gives the output is a second-order differential equation of the form

$$\frac{d^2y(t)}{dt^2} + \frac{dy(t)}{dt} + 5y(t) = 3 \quad t \geq 0$$

$$s^2 + s + 5 = 0 \Rightarrow s_1 = -0.5 + j\sqrt{4.75}, s_2 = -0.5 - j\sqrt{4.75}$$

$$y(t) = B_1 e^{-\frac{t}{2}} \cos(\sqrt{4.75}t) + B_2 e^{-\frac{t}{2}} \sin(\sqrt{4.75}t) + \frac{3}{5} \quad t \geq 0$$

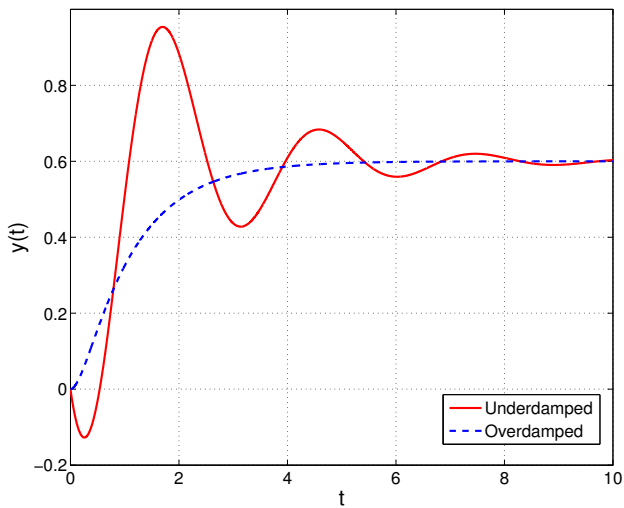Using the initial conditions we find  $B_1 = \frac{-3}{5}$  and  $B_2 = \frac{3}{10\sqrt{4.75}}$  (check!).



The response of this system to the unit step is said to be *underdamped*.

**Case**  $\alpha = \omega$ :  $s_1 = s_2 = -\alpha$

$$y(t) = (D_1 + D_2(t - t_0))e^{-\alpha(t-t_0)} \quad t \geq t_0,$$

where  $D_1$  and  $D_2$  can be found using the initial conditions.

## Exercise

Let  $x(t) = 3u(t)$  be the input signal to a system defined by the following input/output relationship:

$$\frac{d^2y(t)}{dt^2} + 2\sqrt{5}\frac{dy(t)}{dt} + 5y(t) = x(t),$$

where  $y(t)$  is the output signal. If we know that  $y(0) = 0$  and  $\frac{dy(t)}{dt}|_{t=0} = 0$ , compute and plot  $y(t)$ .

**Sol.**


For  $t \geq 0$ , the equation that gives the output is a second-order differential equation of the form

$$\frac{d^2y(t)}{dt^2} + 2\sqrt{5}\frac{dy(t)}{dt} + 5y(t) = 3 \quad t \geq 0$$

$$s^2 + 2\sqrt{5}s + 5 = 0 \Rightarrow s_1 = s_2 = -\sqrt{5}$$

$$y(t) = (D_1 + D_2t)e^{-\sqrt{5}t} + \frac{3}{5} \quad t \geq t_0$$

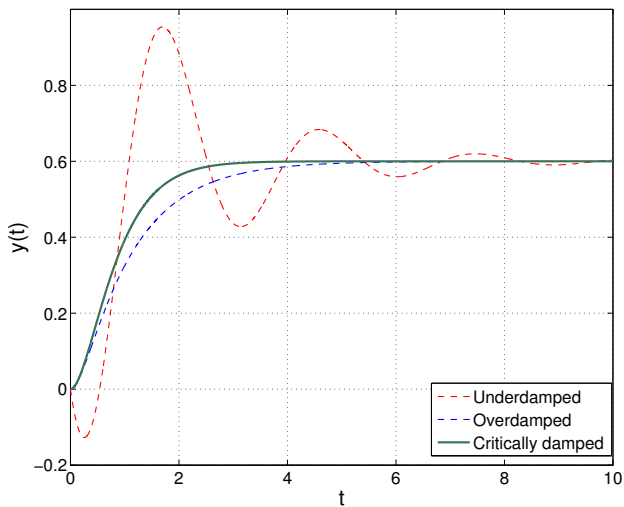Using the initial conditions we find  $D_1 = \frac{-3}{5}$  and  $D_2 = \frac{3}{\sqrt{5}}$ .



The response of this system to the unit step is said to be *critically damped*.




# Index

1 General solution of the Second-order differential equation

2 RLC circuits


3 RLC circuits as systems (filters)

## Example

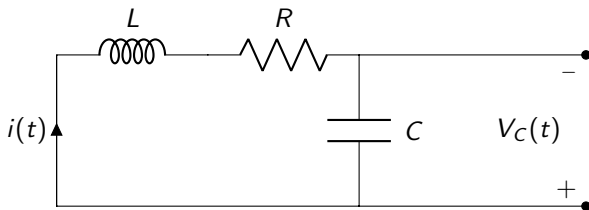

If  $i(0) = i_0$  and  $\frac{\partial i(t)}{\partial t} \big|_{t=0} = i'_0$ , determine the differential equation for the current  $i(t)$  for  $t \geq 0$ .

Sol.

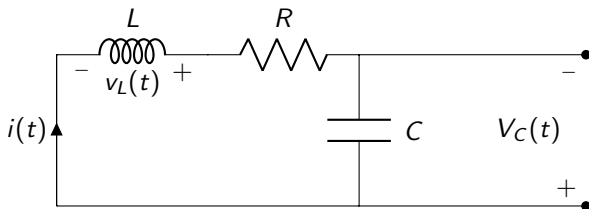

KVL in the loop:

$$v_L(t) + i(t)R + V_C(t) = 0$$

We express all terms as a function of  $i(t)$ :

$$v_L(t) = L \frac{\partial i(t)}{\partial t}$$

$$v_C(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

Thus

$$L \frac{\partial i(t)}{\partial t} + i(t)R + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = 0$$

This equation can be transformed into a second order differential equation by computing the time-derivative at both sides of the equation...

$$L \frac{\partial^2 i(t)}{\partial t^2} + \frac{\partial i(t)}{\partial t} R + \frac{1}{C} i(t) = 0$$

To find the solution for  $i(t)$   $t \geq 0$  using our "recipe", we divide by  $L$  so the coefficient for  $\frac{\partial^2 i(t)}{\partial t^2}$  is one...

$$\frac{\partial^2 i(t)}{\partial t^2} + \frac{R}{L} \frac{\partial i(t)}{\partial t} + \frac{1}{LC} i(t) = 0$$

$$\frac{d^2 y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_0^2 y(t) = \gamma, \quad s^2 + 2\alpha s + \omega_0^2 = 0, \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


We identify terms

$$\frac{\partial^2 i(t)}{\partial t^2} + \frac{R}{L} \frac{\partial i(t)}{\partial t} + \frac{1}{LC} i(t) = 0 \quad \Rightarrow \quad \omega_0^2 = \frac{1}{LC}, \quad 2\alpha = R/L.$$

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$


- $R > 2\sqrt{\frac{L}{C}} \rightarrow$  real (negative) roots. Overdamped solution.
- $R < 2\sqrt{\frac{L}{C}} \rightarrow$  complex roots. Underdamped solution.
- $R = 2\sqrt{\frac{L}{C}} \rightarrow$  2 equal roots. Critically damped solution.
- $R = 0 \rightarrow$  Oscillation.

## Example

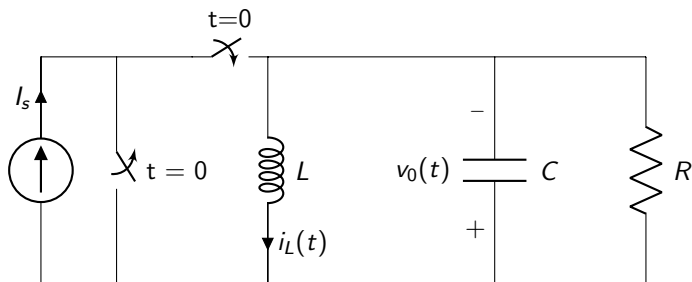

Determine the differential equation for the current  $i_L(t)$  for  $t \geq 0$ .

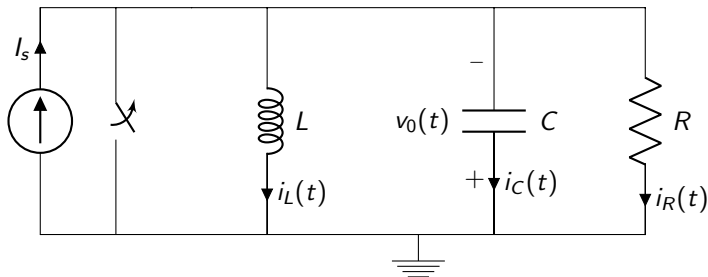Determine the differential equation for the voltage  $v_0(t)$  for  $t \geq 0$ .



$$\text{KCL: } I_s = i_L(t) + i_C(t) + i_R(t)$$

- Inductor:  $v_0(t) = L \frac{\partial i_L(t)}{\partial t}$
- Resistor:  $i_R(t) = v_0(t)/R = \frac{L}{R} \frac{\partial i_L(t)}{\partial t}$
- Capacitor:  $i_C(t) = C \frac{\partial v_0(t)}{\partial t} = CL \frac{\partial^2 i_L(t)}{\partial^2 t}$

$$\frac{d^2 y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_0^2 y(t) = \gamma, \quad s^2 + 2\alpha s + \omega_0^2 = 0, \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Therefore

$$CL \frac{\partial^2 i_L(t)}{\partial t^2} + \frac{L}{R} \frac{\partial i_L(t)}{\partial t} + i_L(t) = I_s$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC}, 2\alpha = \frac{1}{RC}, \gamma = \frac{I_s}{CL}$$


$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\frac{1}{4(RC)^2} - \frac{1}{LC}}$$

- $R < \frac{1}{2} \sqrt{\frac{L}{C}} \rightarrow$  real (negative) roots. Overdamped solution.
- $R > \frac{1}{2} \sqrt{\frac{L}{C}} \rightarrow$  complex roots. Underdamped solution.
- $R = \frac{1}{2} \sqrt{\frac{L}{C}} \rightarrow$  2 equal roots. Critically damped solution.
- $R = \infty \rightarrow$  Oscillation.



## Auxiliary conditions


We need  $i_L(0^+)$  and  $\frac{\partial i_L(t)}{\partial t}|_{t=0^+}$ . If the circuit has been operating for a long time before the switch is open, then the equivalent circuit is

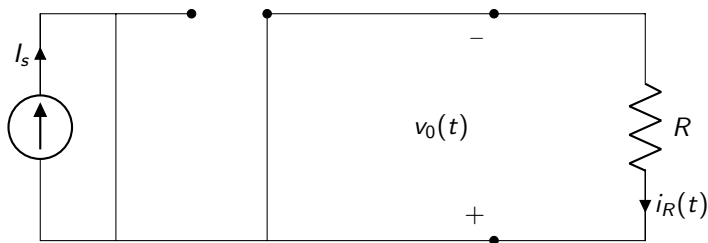

Therefore,  $i_L(0^-) = i_L(0^+) = 0$  A and  $v_0(0^-) = v_0(0^+) = 0$  V. Since  $v_0(t) = L \frac{\partial i_L(t)}{\partial t}$ , this means

$$\frac{\partial i_L(t)}{\partial t}|_{t=0^+} = 0 \quad \text{A/s}$$



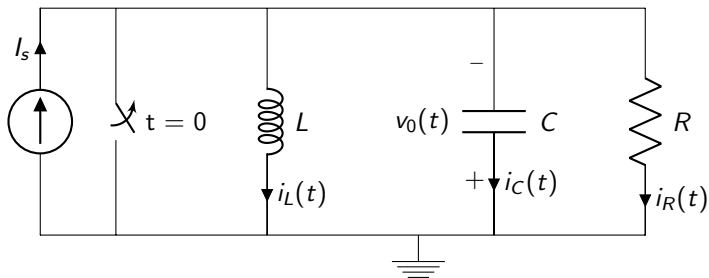

$$\text{KCL: } I_s = i_L(t) + i_C(t) + i_R(t)$$

- Resistor:  $i_R(t) = v_0(t)/R$
- Capacitor:  $i_C(t) = C \frac{\partial v_0(t)}{\partial t}$
- Inductor:  $i_L(t) = \frac{1}{L} \int_{-\infty}^t v_0(\tau) d\tau$

Therefore

$$I_s = \frac{1}{L} \int_{-\infty}^t v_0(\tau) d\tau + C \frac{\partial v_0(t)}{\partial t} + \frac{1}{R} v_0(t)$$

If we compute the time-derivative at both sides of the equation

$$\frac{\partial^2 v_0(t)}{\partial t^2} + \frac{1}{RC} \frac{\partial v_0(t)}{\partial t} + \frac{1}{LC} v_0(t) = 0$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\frac{1}{4(RC)^2} - \frac{1}{LC}}$$

- $R < \frac{1}{2} \sqrt{\frac{L}{C}} \rightarrow$  real (negative) roots. Overdamped solution.
- $R > \frac{1}{2} \sqrt{\frac{L}{C}} \rightarrow$  complex roots. Underdamped solution.
- $R = \frac{1}{2} \sqrt{\frac{L}{C}} \rightarrow$  2 equal roots. Critically damped solution.
- $R = \infty \rightarrow$  Oscillation.


# Index

1 General solution of the Second-order differential equation

2 RLC circuits

3 RLC circuits as systems (filters)

## RLC circuits as systems

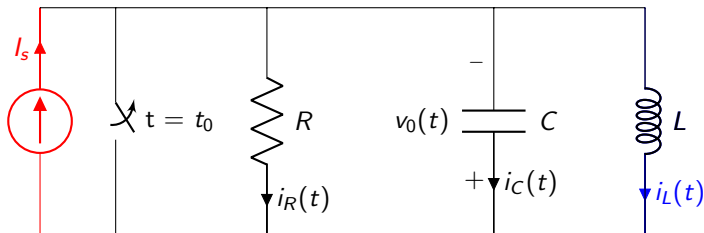

Differential equation for  $i_L(t)$ :

$$\frac{\partial^2 i_L(t)}{\partial^2 t} + \frac{1}{RC} \frac{\partial i_L(t)}{\partial t} + \frac{1}{L} i_L(t) = \frac{I_s}{LC} u(t - t_0)$$

with auxiliary conditions  $i_L(t_0) = A$ ,  $\frac{\partial i_L(t)}{\partial t} \big|_{t=t_0} = B$

We can consider  $I_s u(t - t_0)$  as the **input** and  $i_L(t)$  as the **output** of a system that is implemented by the RLC circuit. These systems are called **filters**.

## Filters

The **system** input/output relationship is given by the differential equation and the auxiliary conditions.

We can characterize the system using the properties defined for systems in the first part of the course. In particular, we will discuss the linearity, time-invariance and causality properties of the filter.

## Linearity

If we put an input current  $i_1$  in the source, we will observe a current in the inductor (system output)  $i_1(t)$  such that:

$$\frac{\partial^2 i_1(t)}{\partial^2 t} + \frac{1}{RC} \frac{\partial i_1(t)}{\partial t} + \frac{1}{L} i_1(t) = \frac{I_1}{LC} u(t - t_0)$$

with auxiliary conditions  $i_1(t_0) = A$ ,  $\frac{\partial i_1(t)}{\partial t} \big|_{t=t_0} = B$

If we consider a different input  $i_2$ , the new output current  $i_2(t)$  verifies

$$\frac{\partial^2 i_2(t)}{\partial^2 t} + \frac{1}{RC} \frac{\partial i_2(t)}{\partial t} + \frac{1}{L} i_2(t) = \frac{I_2}{LC} u(t - t_0)$$

with auxiliary conditions  $i_2(t_0) = A$ ,  $\frac{\partial i_2(t)}{\partial t} \big|_{t=t_0} = B$



If we consider an input that is the linear combination of the two former inputs  $i_3 = ai_1 + bi_2$  the new output  $i_3(t)$  is such that

$$\begin{aligned} \frac{(ai_1 + bi_2)}{LC} u(t - t_0) &= a \left\{ \frac{\partial^2 i_1(t)}{\partial^2 t} + \frac{1}{RC} \frac{\partial i_1(t)}{\partial t} + \frac{1}{L} i_1(t) \right\} + \\ &\quad b \left\{ \frac{\partial^2 i_2(t)}{\partial^2 t} + \frac{1}{RC} \frac{\partial i_2(t)}{\partial t} + \frac{1}{L} i_2(t) \right\} \\ &= \frac{\partial^2 (ai_1(t) + bi_2(t))}{\partial^2 t} + \frac{1}{RC} \frac{\partial (ai_1(t) + bi_2(t))}{\partial t} + \frac{1}{L} (ai_1(t) + bi_2(t)) \end{aligned}$$

Hence, the output is  $i_3(t) = ai_1(t) + bi_2(t)$ .

But we have to see what happens with the auxiliary conditions.

## Filter linearity: auxiliary conditions

The current  $i_3(t)$  must verify

$$\begin{aligned} i_3(t_0) &= A \\ \frac{\partial i_3(t)}{\partial t} \Big|_{t=t_0} &= B \end{aligned} \Rightarrow \begin{aligned} a i_1(t_0) + b i_2(t_0) &= A \\ \frac{\partial (a i_1(t) + b i_2(t))}{\partial t} \Big|_{t=t_0} &= B \end{aligned}$$

On the other hand

$$\begin{aligned} a i_1(t_0) + b i_2(t_0) &= aA + bA \\ \frac{\partial (a i_1(t) + b i_2(t))}{\partial t} \Big|_{t=t_0} &= aB + bB \end{aligned}$$

Putting all together

$$\begin{aligned} A &= (a + b)A \\ B &= (a + b)B \end{aligned}$$

which has to be true for any  $a, b$ , hence  $A = B = 0$ .

Linearity condition for a filter

Null auxiliary conditions!

## Time Invariancy

- $i_L(t)$  is the output when the input is  $I_s u(t - t_0)$ .
- If we close the switch at  $t_1 > t_0$ , we are essentially delaying the input:  $I_s u(t - t_1)$ .
- For this new input, we know the solution is automatically shifted to  $t_1$  (the exponential solution will depend on  $(t - t_1)$ ).
- However, the auxiliary conditions have to be defined at  $t_1$ !!! Otherwise, the system is not time-invariant!

### Filter time-invariance condition

Auxiliary conditions must be referred to the instant at which the input is activated (auxiliary conditions are initial conditions).

# Causality

## Filter causality condition

Auxiliary conditions are **null initial conditions**.

- This guarantees that the output signal  $i_L(t)$  is zero as long as the input hasn't been activated.